

# Radio Frequency Integrated Circuits and Systems Laboratory -RFICS Lab-

Integrated Circuits Design For Communications

## DESIGN OF DIFFERENTIAL AMPLIFIER WITH MOS LOAD


### -MINIPROJECT 1-

Student: Le Truong Quoc

☐ Work plan for this week

	Works	Results	Progress
1	Design of Differential pair with diode-connected	100%	Finish
2	Design of Differential pair with PMOS source follower	100%	Finish

# Experiment 1

 


*Differential pair with diode-connected*


SPECIFICATIONS	
Voltage Supply	1.2 V
GAIN	7dB
Unity Gain Bandwidth	130MHz
Power Consumption	<0.15mW
Output Voltage	>450mV
Load Capacitance ( $C_L$ )	1pF
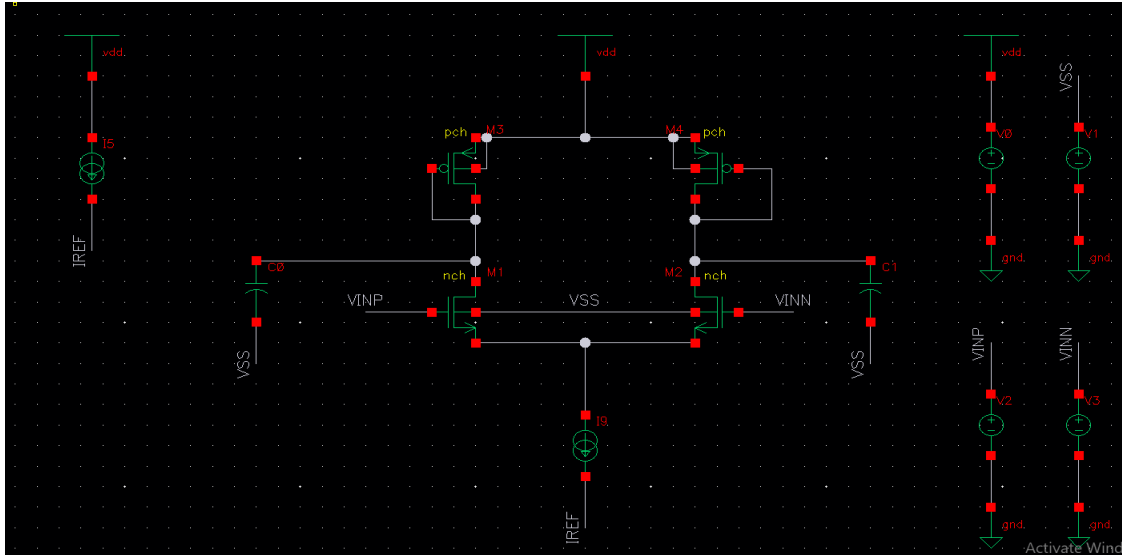
## Requirements:

- Design of differential pair with diode-connected with the specifications as shown in the table above by gm/Id methodology.
- Replace the source current by the current mirrors.
- What can you do to achieve higher gain or bandwidth, and what are the trade-offs in this scenario?
- Compare this structure to the differential pair with current source loads.



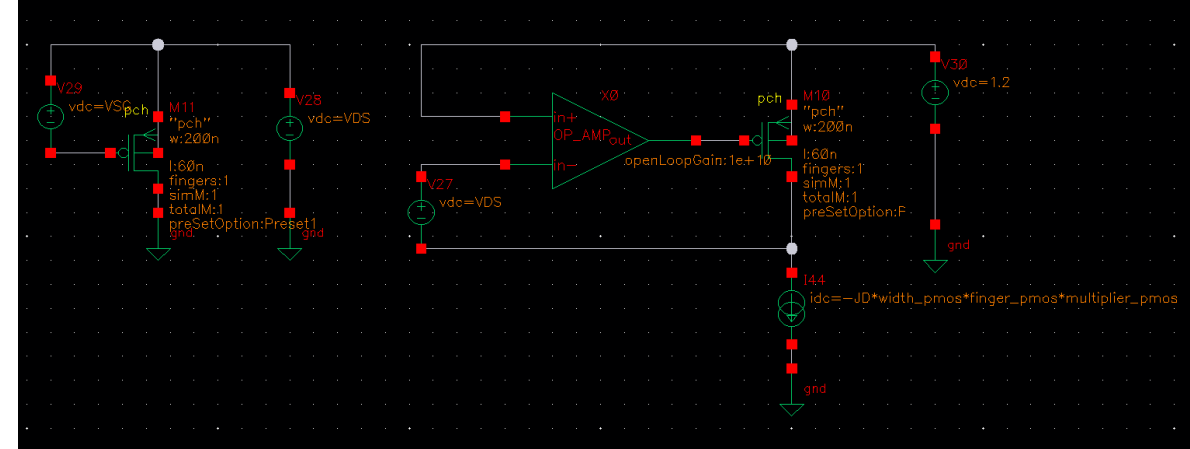The testbench of differential pair with diode-connected loads



The gmID testbench for PMOS

- Use the gmID testbench as the previous lab for design.
- Consider related expressions (gain, unity gain bandwidth,...) and build them into the ADEL gmID testbench to choose the parameters of a transistor for achieve the specifications. (Refer to Chapter 4 – 6 in AICD\_Lectures).
- *Note that: the transistor can operate in the region 3 of this design (not high frequency).*

**Your report must be shown:**


- **Your design flow and the outcomes of the simulation (comments & review).**
- **How do you choose the parameters ( $V_{DS}$ ,  $V_{bias}$ ,  $I_d$ , length, width,...) for design? Why?**

# Experiment 1

The design flow of this problem is as follows:

First, we can calculate the ranges for  $V_{SD}$ ,  $V_{SG}$ ,  $V_{DS}$ ,  $V_{GS}$ . From these, we can determine the corresponding values based on the parameters provided in the table, which will be presented in the next slide.

 1. Using the testbench of the PMOS, find the  $gm_p$ ,  $rout_p$  and find  $gm/id$ ,  $J_D$  versus  $V_{SG}$ . From that, determine the corresponding width.
2. From the values of  $gm_p$  and  $rout_p$ , write the function  $A_v$  versus  $I_D$  and find the value of  $V_{GS}$  in testbench of the NMOS.
3. From the formula  $GBW = \frac{gm_N}{2\pi C_L}$  we can find  $gm_N$ . We can plot  $gm/id$  and  $J_D$  versus  $V_{GS}$  to determine the width.
4. Calculate the  $V_{IN\_DC}$  of the circuit and apply the values of the NMOS and PMOS to the circuit. Plotting the gain.




*Differential pair with diode-connected*

# Experiment 1


Based on the parameters in the table:

We have  $P < 0.15 \text{ mW} \Rightarrow P/U < 0.15/U \Rightarrow I < 0.125 \text{ mA} \Rightarrow$   
choose  $I = 100 \mu\text{A}$  (total current).

 - $I_{D1} = I_{D2} = 50 \mu\text{A}$
- $V_{out} > 450 \text{ mV} \Rightarrow V_{DD} - V_{SD} > 450 \text{ mV} \Rightarrow V_{SD} < 750 \text{ mV}$
- We choose  $V_{out} = 480 \text{ mV}$ , so  $V_{SD} = V_{SG} = 720 \text{ mV}$





*Differential pair with diode-connected*

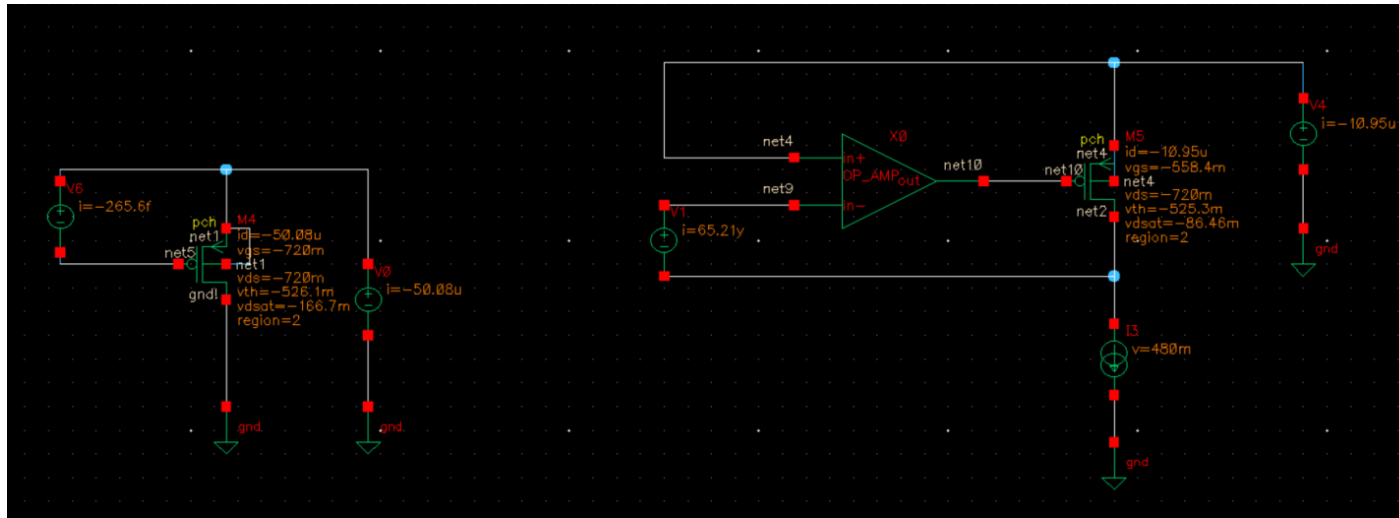

*The gm<sub>id</sub> testbench for PMOS*



# Experiment 1

  

Based on the graph, we have  $g_{m_p} = 348.88\mu$ ,  $r_{out_p} = 24.44K$  as  $V_{SG} = 720mV$

As increasing the length,  $V_{TH}$  will decrease, which reduces  $g_{m_p}$ , increases  $r_{out_p}$ , and can reduce the overall gain of the circuit. Since the length affects the  $V_{TH}$  of the PMOS, in this case, we fix the length at 60nm (same the values from the previous lab) , with  $V_{TH}$  approximately 526 mV.

# Experiment 1

  


Based on the graph, we have  $gm/id = -6.906$ ;  $J_D = -45.08182$  as  $V_{SG} = 720\text{mV}$

We need to keep  $I_D = 50\mu\text{A}$  and find the value of  $W$  to achieve the desired gain
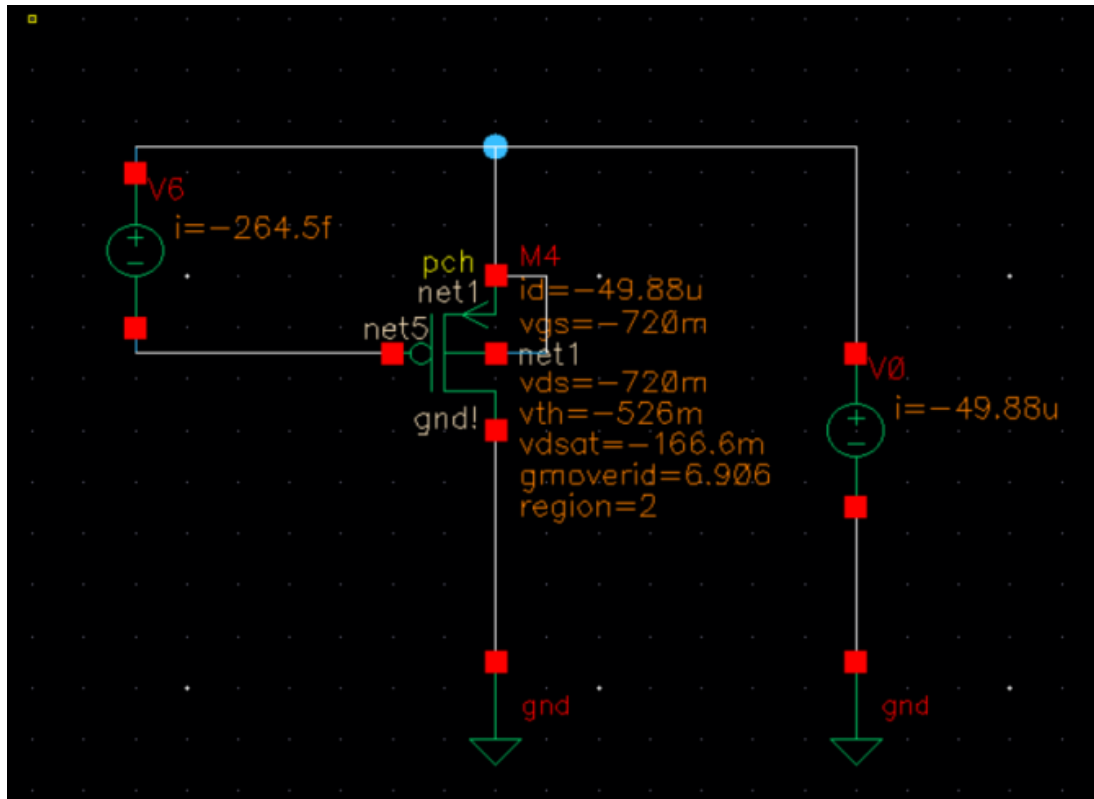
$$\text{Have: } J_D = \frac{I_D}{W} \Rightarrow W = \frac{I_D}{J_D} = \frac{50\mu}{-45.08182} \approx 1.093\mu$$





DC Operating point check

With  $V_{SD} = V_{SG} = 720mV$ ,  $L = 60nm$ ,  $W = 1.093u$ . We found the  $I_D \approx 50uA$  in the testbench.

## For NMOS transistors

As the length increases,  $V_{TH}$  decreases. For NMOS, we should choose a smaller value to make it easier to adjust the width, because if the width is too large when the length is high, the gain decreases at high frequencies due to the increased parasitic capacitances.

We have:

$$\omega_p = [(r_{O1} || r_{O2}) C_L]^{-1}$$


$$|A_0| = g_{m1} (r_{O1} || r_{O2})$$

Unity gain band-width: As circuit has dominant pole:  $GBW = \omega_u$

$$\begin{aligned} \omega_u &= \sqrt{A_0^2 - 1} \omega_p \\ &\approx A_0 \omega_p \end{aligned}$$

We have Unity gain band-width = 130MHz

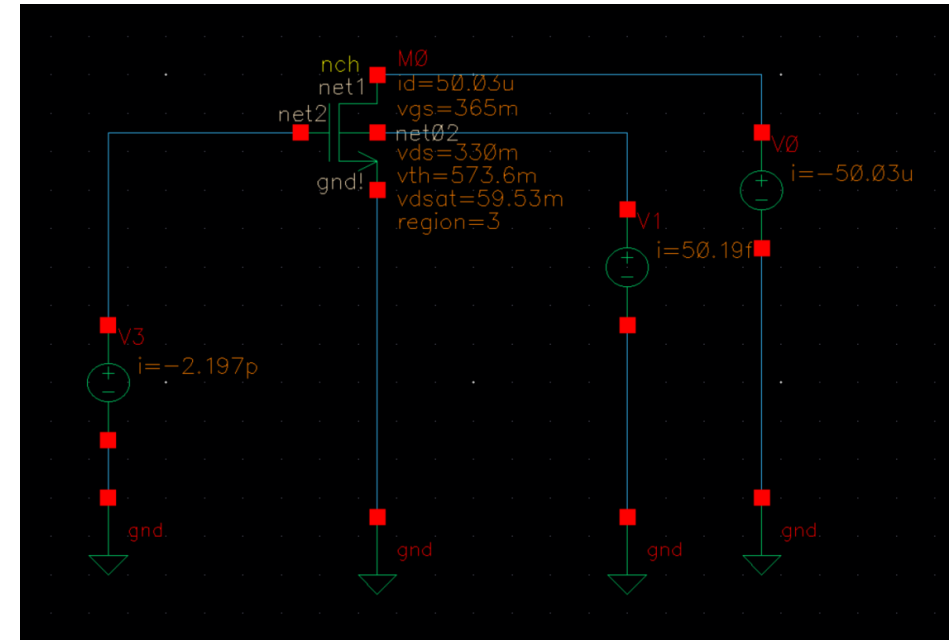
$$GBW = \frac{g_{mN}}{2\pi C_L} \leftrightarrow 130MHz = \frac{g_{mN}}{2\pi \times 1pF} \rightarrow g_{mN} = 8,168 \times 10^{-4} \text{ S (minimum value of NMOS)}$$



The gmId testbench for NMOS

# Experiment 1

## For NMOS transistors

 

We have:  $g_{m_P} = 345.88\mu$ ;  $r_{out_P} = 24.44K \Rightarrow$   
 $\frac{1}{g_{m_P}} // r_{out_P} = 2585.34\Omega$   
And:


$$A_v = -g_{m_N} \left( \frac{1}{g_{m_P}} // r_{out_P} // r_{out_N} \right)$$

$$A_v@50\mu A = (g_{m@50\mu A})(R_D // (r_{o@50\mu A}))$$

We write the  $a_v$  function based on the values calculated at  $I_D = 50 \mu A$ , at  $A_v = 7dB$  as  $V_{GS} \approx 365mV$ .

Function:  $((\text{getData}("M3:gm" ?result "dc") / \text{getData}("M3:id" ?result "dc")) * 5e-05) * ((2585 * \text{getData}("M3:rout" ?result "dc") * \text{getData}("M3:id" ?result "dc")) / 60u) / (2585 + \text{getData}("M3:rout" ?result "dc") * \text{getData}("M3:id" ?result "dc") / 50u))$

# Experiment 1

 


Graph of  $J_D$  (left) and  $gm/id$  (right) versus  $V_{GS}$

Based on the graph, we have  $gm/id = 21.7921\text{ S}$ ;  $J_D = 887.499\text{ m A/m}$  as  $V_{SG} = 365\text{ mV}$ .

We need to keep  $I_D = 50\text{ uA}$  and find the value of  $W$  to achieve the desired gain.

$$\text{Have: } J_D = \frac{I_D}{W} \Rightarrow W = \frac{I_D}{J_D} = \frac{50\text{ u}}{887.499\text{ m}} \approx 69.73\text{ u}$$

# Experiment 1

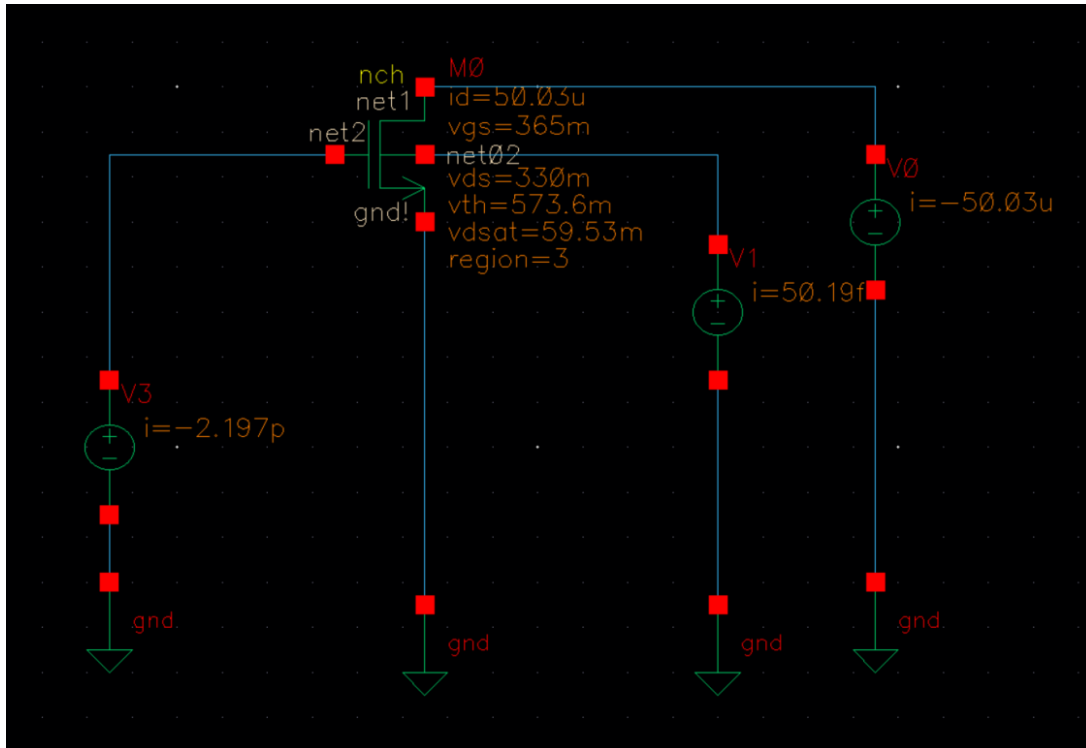

DC Operating point check

Name	
1 vsb	150m
2 finger_nmos	1
3 length_nmos	60n
4 multiplier_nmos	1
5 vds	330m
6 vgs	365m
7 width_nmos	71.3u

Design variables

We choose  $V_{ISS} = 150mV$  (same in previous lab), bias voltage for NMOS

$$V_{out} = V_{DS} + V_{ISS} ;$$


$$\Rightarrow V_{DS} = V_{out} - V_{ISS} = 0.48 - 0.15 = 0.35mV$$

With these values, the NMOS operates in region 3 (which is still allowed in this project).


With  $V_{DS} = 0.35mV$ ;  $V_{GS} = 365mV$ ,  $L = 60nm$ ,  $W = 71.3u$ .

We found the  $I_D \approx 50\mu A$  in the testbench.

# Experiment 1

 

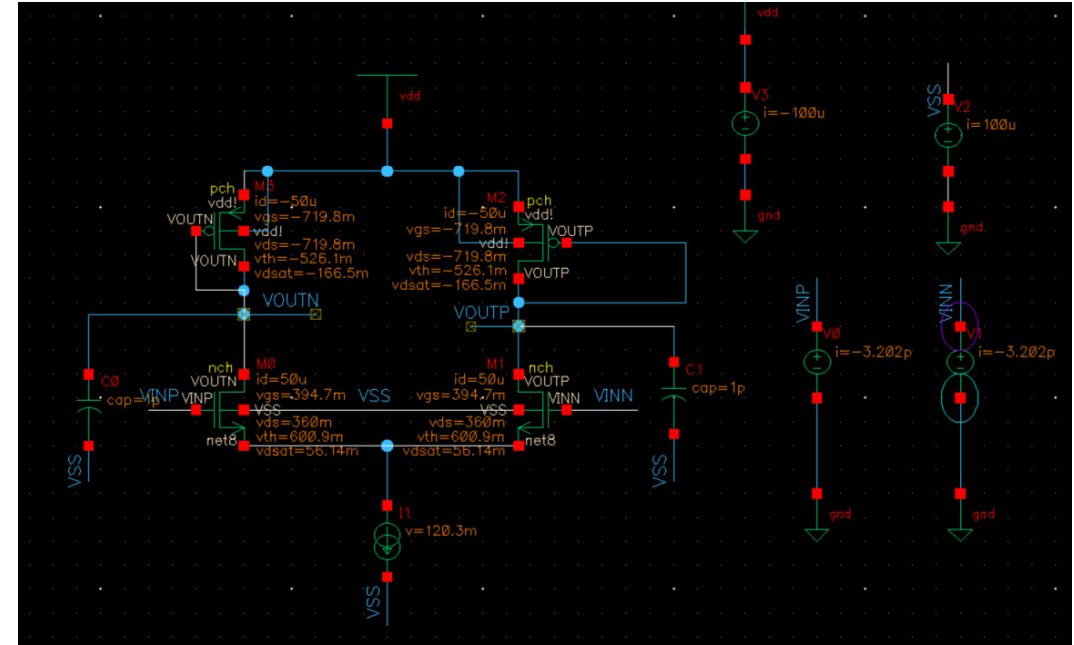Frequency response of *differential pair with diode-connected*




## DC Operating point check

We have:  $V_{INP} = V_{INN} = V_{GS} + V_{ISS}$   
 $= 0.365 + 0.15 = 0.515mV$

Design Variables		
	Name	
1	length_nmos	60n
2	length_pmos	60n
3	width_nmos	71.3u
4	width_pmos	1.095u
5	VINN	515m
6	VINP	515m

# Experiment 1

## For PMOS transistors

 

We also use the gm/ID methodology to continue finding the values for NMOS and PMOS as we did before




- $V_{out} > 450m \Rightarrow V_{DD} - V_{SD} > 450mV \Rightarrow V_{SD} < 750mV$
- We choose  $V_{out} = 500mV$ , so  $V_{SD} = V_{SG} = 700mV$

Based on the graph, we have  $gm_p = 362.87u$ ,  $rout_p = 23.67K$  as  $V_{SG} = 700mV$

As increasing the length,  $V_{TH}$  will decrease, which reduces  $gm_p$ , increases  $rout_p$ , and can reduce the overall gain of the circuit. Since the length affects the  $V_{TH}$  of the PMOS, in this case, we fix the length at 60nm (same the values from the previous lab) , with  $V_{TH}$  approximately 530 mV.



# Experiment 1

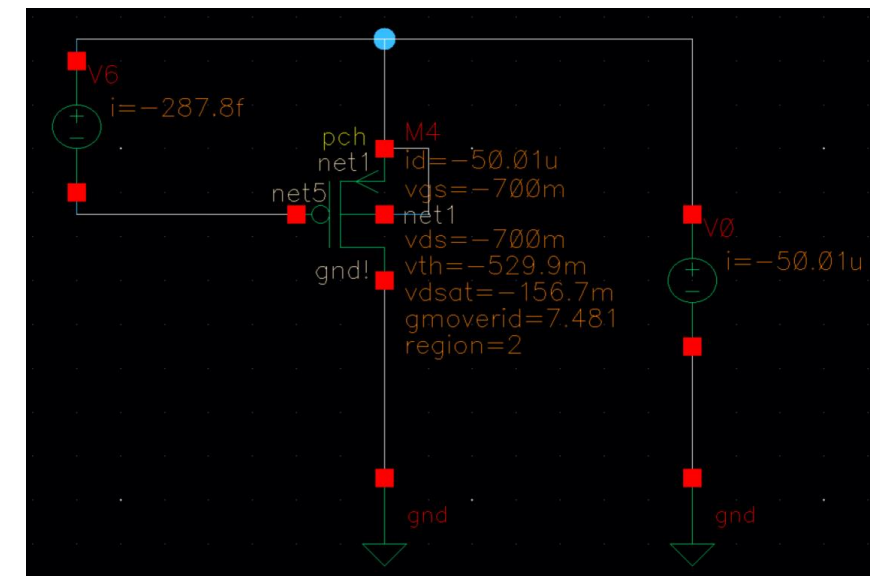  

DC Operating point check

Based on the plot, we have  $gm/id = -7.487$ ;  $J_D =$

$-39.4444$  as  $V_{SG} = 700mV$

We need to keep  $I_D = 50uA$  and find the value of  $W$  to achieve the desired gain


$$\text{Have: } J_D = \frac{I_D}{W} \Rightarrow W = \frac{I_D}{J_D} = \frac{50u}{39.4444} \approx 1.301u$$

Name	Value
1 VSD	700m
2 VSG	700m
3 finger_pmos	1
4 length_pmos	60n
5 multiplier_pmos	1
6 width_pmos	1.303u



# Experiment 1

## For NMOS transistors

 

$$Av@50\mu A = (gm@50\mu A)(RD//(ro@50\mu A))$$

We write the  $av$  function based on the values calculated at  $I_D = 50 \mu A$ , at  $Av = 7dB$  as  $V_{GS} \approx 336mV$ .


Function:  $((getData("M3:gm" ?result "dc") / getData("M3:id" ?result "dc")) * 5e-05) * ((2585 * getData("M3:rout" ?result "dc") * getData("M3:id" ?result "dc") / 60u) / (2585 * getData("M3:rout" ?result "dc") * getData("M3:id" ?result "dc") / 50u))$

We have:  $gm_P = 362.87\mu$ ;  $rout_P = 23.67K \Rightarrow \frac{1}{gm_P} // rout_P = 2468.41K$

And:

$$Av = -gm_N \left( \frac{1}{gm_P} // rout_P // rout_N \right)$$

# Experiment 1

 


Based on the graph, we have  $gm/id = 231071 \text{ S}$ ;  $J_D = 453.083 \text{ m A/m}$  as  $V_{GS} = 336 \text{ mV}$ .

We need to keep  $I_D = 50 \mu\text{A}$  and find the value of  $W$  to achieve the desired gain.

$$\text{Have: } J_D = \frac{I_D}{W} \Rightarrow W = \frac{I_D}{J_D} = \frac{50 \mu}{453.083 \text{ m}} \approx 133.3 \mu$$

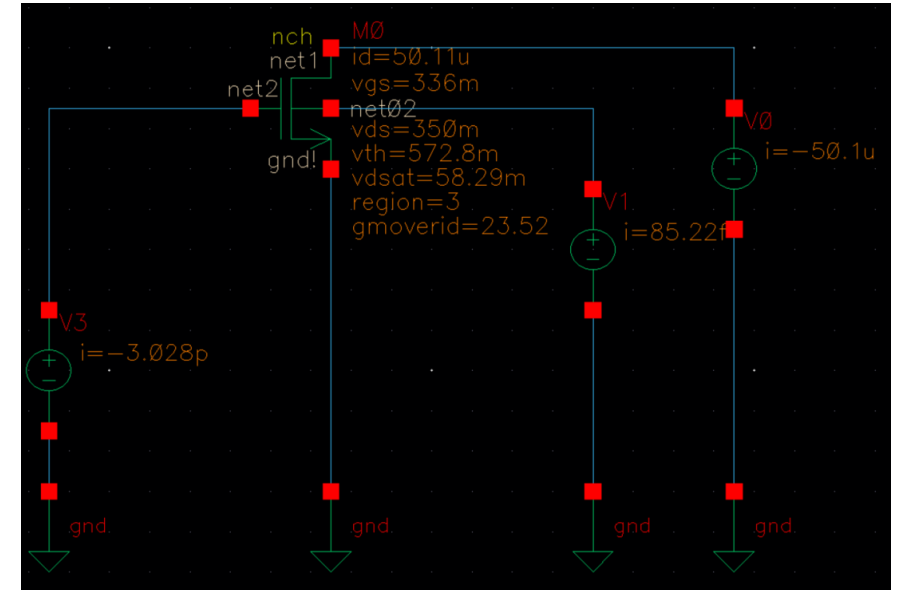We use this plot to find the most accurate value for  $W$  when  $I_D = 50 \mu$




With these values, the NMOS operates in region 3 (which is still allowed in this project).

With  $V_{DS} = 0.35 \text{ mV}$ ;  $V_{GS} = 336 \text{ mV}$ ,  $L = 60 \text{ nm}$ ,  $W = 133.6 \mu$ . We found the  $I_D \approx 50 \mu\text{A}$  in the testbench

Name	Value
finger_nmos	1
length_nmos	60n
multiplier_nmos	1
vds	350m
vgs	336m
vsb	150m
width_nmos	133.6u

# Experiment 1

 


Based on the graph, we have  $gm/id = 231071 \text{ S}$ ;  $J_D = 453.083 \text{ m A/m}$  as  $V_{GS} = 336 \text{ mV}$ .

We need to keep  $I_D = 50 \mu\text{A}$  and find the value of  $W$  to achieve the desired gain.

$$\text{Have: } J_D = \frac{I_D}{W} \Rightarrow W = \frac{I_D}{J_D} = \frac{50 \mu}{453.083 \text{ m}} \approx 133.3 \mu$$

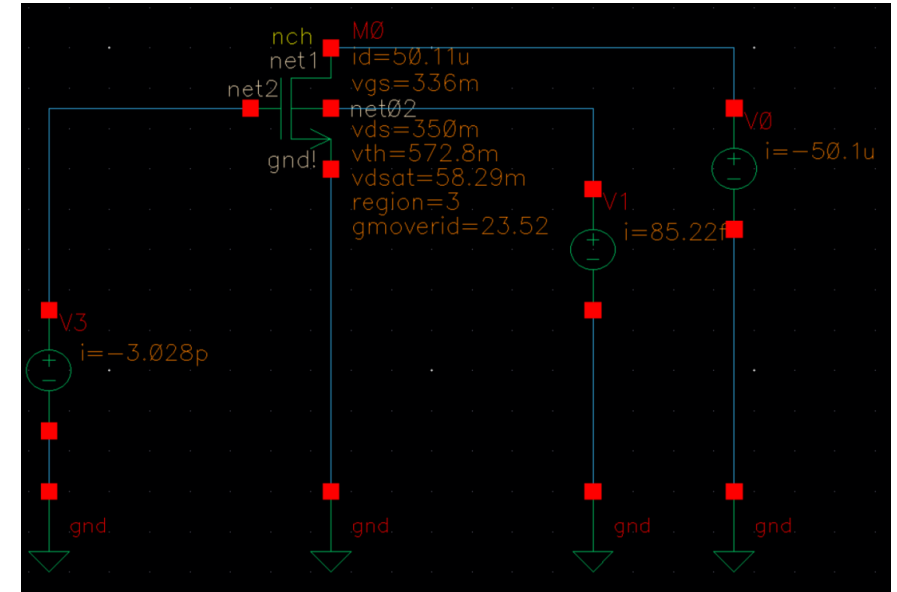We use this plot to find the most accurate value for  $W$  when  $I_D = 50 \mu$




With these values, the NMOS operates in region 3 (which is still allowed in this project).


With  $V_{DS} = 0.35 \text{ mV}$ ;  $V_{GS} = 336 \text{ mV}$ ,  $L = 60 \text{ nm}$ ,  $W = 133.6 \mu$ . We found the  $I_D \approx 50 \mu\text{A}$  in the testbench

Name	Value
finger_nmos	1
length_nmos	60n
multiplier_nmos	1
vds	350m
vgs	336m
vsb	150m
width_nmos	133.6u

# Experiment 1

 

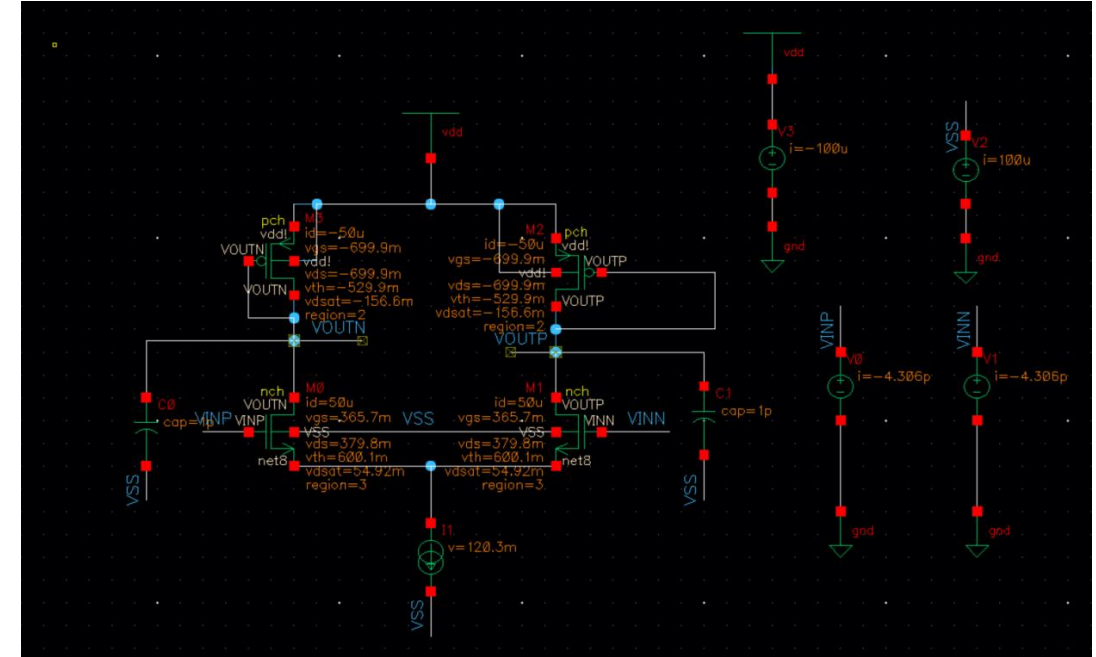Frequency response of *differential pair with diode-connected*





DC Operating point check

As reducing  $V_{ISS}$ , the gate-source voltage  $V_{GS}$  of the NMOS transistors will decrease. If  $V_{GS}$  decreases too much, it might fall below the threshold voltage  $V_{TH}$  of the NMOS, causing the transistors to operate in the subthreshold region. When  $V_{ISS}$  is reduced, you may need to adjust other circuit components to compensate for the reduced  $g_m$  and changes in transistor sizing, which could increase parasitic capacitance and impact high-frequency performance. However, here we choose  $V_{out}$  higher than the previous test so the headroom will be better.

$$\text{We have: } V_{INP} = V_{INN} = V_{GS} + V_{ISS} = 0.336 + 0.15 = 0.486mV$$

	Name	Val
1	length_nmos	60n
2	length_pmos	60n
3	width_nmos	133.6u
4	width_pmos	1.303u
5	VINN	486m
6	VINP	486m

## Change length of NMOS

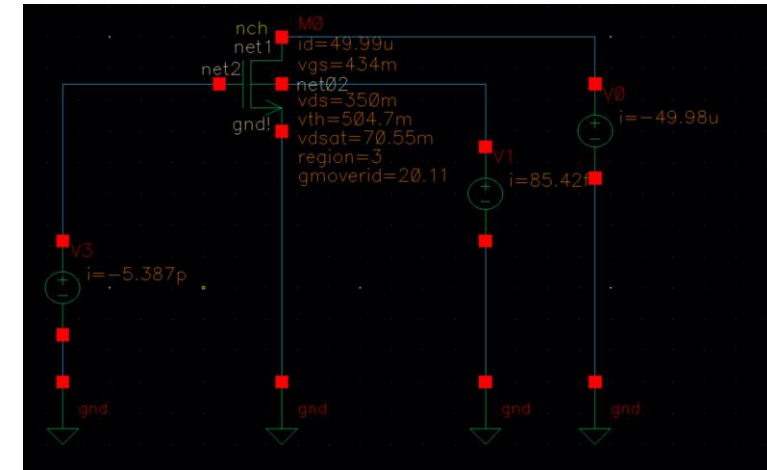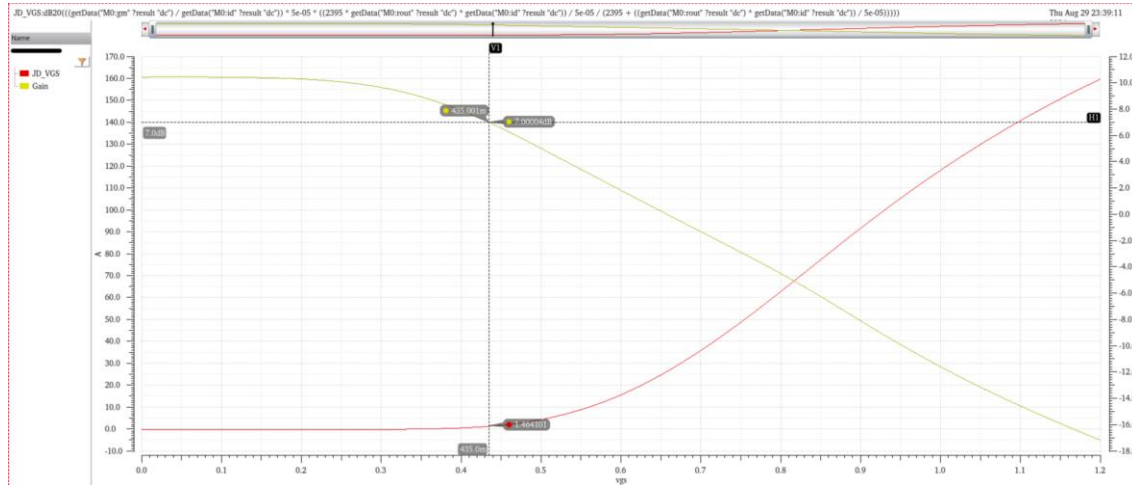


Design Variables	
Name	Value
1 finger_nmos	1
2 length_nmos	200n
3 multiplier_nmos	1
4 vds	350m
5 vgs	434m
6 vsb	150m
7 width_nmos	35.2u

## DC Operating point check for NMOS

Based on the graph, we have  $J_D = 1.4641$  as  $A_v = 7\text{dB}$


$$\text{Have: } J_D = \frac{I_D}{W} \Rightarrow W = \frac{I_D}{J_D} = \frac{50\mu}{1.4641} \approx 34.2\mu\text{M}$$

 Enter the values into the NMOS testbench, then plot JD to find the width such that  $I_D$  in the testbench equals  $50\mu\text{A}$ . We find  $W = 35.2\mu\text{M}$



- When increasing the length while keeping  $I_D = 50\mu\text{A}$  (constant),  $V_{GS}$  must increase, which decreases the transconductance ( $g_m$ ). Increasing the length leads to a decrease in  $\lambda$  and an increase in  $r_{oN}$ . When  $g_m$  decreases and  $r_{oN}$  increases, the decrease in  $g_m$  can significantly reduce the gain. Increasing the length also causes the intrinsic capacitances  $C_{gd}$  and  $C_{db}$  to decrease, which increases the unity bandwidth.



 


As dividing a transistor, the total area remains the same, but the intrinsic capacitance of each finger is smaller. Although the intrinsic capacitance of each individual finger is smaller, the total capacitance of the entire transistor (when all fingers are combined) remains unchanged. Therefore, the unity bandwidth, which depends on the total intrinsic capacitance, does not change significantly. The transconductance of each smaller finger may be lower compared to a larger transistor. The gain decreases from 7.17 dB to 6.8 dB, corresponding to a reduction of approximately 0.37 dB. This reduction occurs because dividing the transistor into fingers can reduce the transconductance of the transistor due to changes in the configuration of the fingers.

### DC Operating point check

 
# Experiment 1

Function:

- $JD (gm/id) nch: waveVsWave(?x (getData("M3:gm" ?result "dc") / getData("M3:id" ?result "dc")) ?y (getData("M3:id" ?result "dc") / (VAR("width_nch") * VAR("finger_nch"))))$
- $v("M2:vth" ?result "dc")$




 
The plot of the  $V_{ov\_gm/id}$  with length = 1u



The plot of the  $V_{TH\_VGS}$  with length = 1u

At  $V_{GS2} = 565$  mV, we know that  $V_{TH} = 555$  mV. With the value of  $V_{TH} = 555$  mV we need to choose  $V_{GS2} > 555$  mV. Besides, we obtain  $V_{DS2} = 120$  mV, so we need to choose  $gm/id$  with  $v_{dsat}$  (overdrive voltage)  $< V_{DS2}$  (to ensure the NMOS operates in the saturation region)

# Experiment 1

  


We choose  $V_{GS} > V_{TH}$  with  $V_{GS} = 565$  mV and  $V_{ov} > V_{GS} - V_{TH}$ . We obtain  $g_{m/id}$  in the range of 10-14.

We choose  $g_{m/id} = 13$ . With this value, we find  $Width\ M1 = 10.83\ \mu m$  and  $J_D = 9.399$  on the plot



# Experiment 1

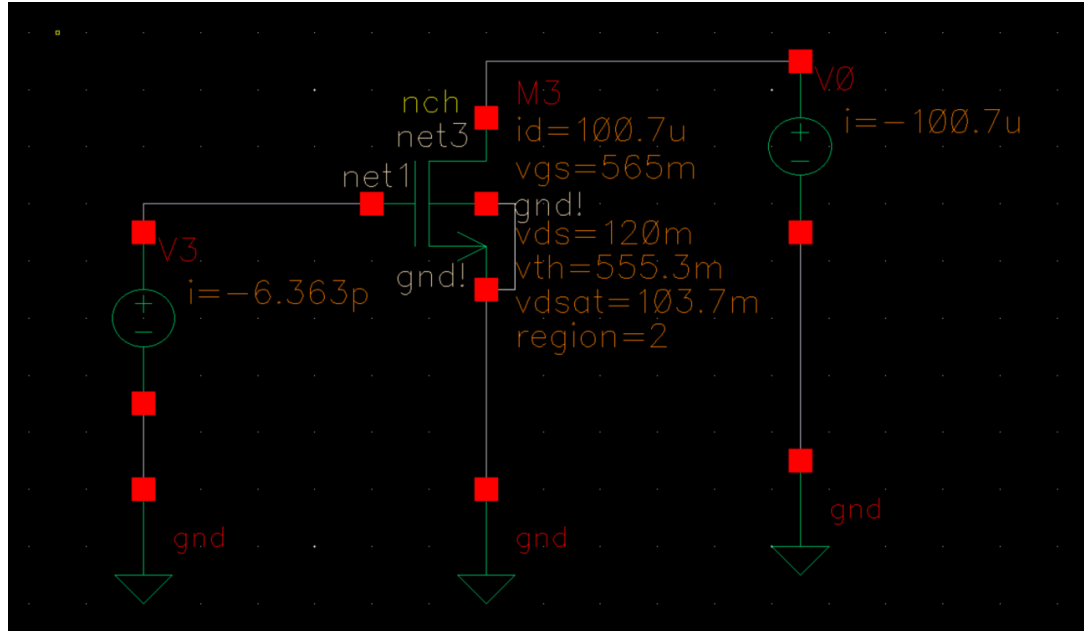


DC operating points of M1 as  $ID = 100\mu A$

Entering the value of design variables after chose by gm/id methodology run DC analysis

Observe the DC operating points, the drain current equal  $100.7\mu$ .

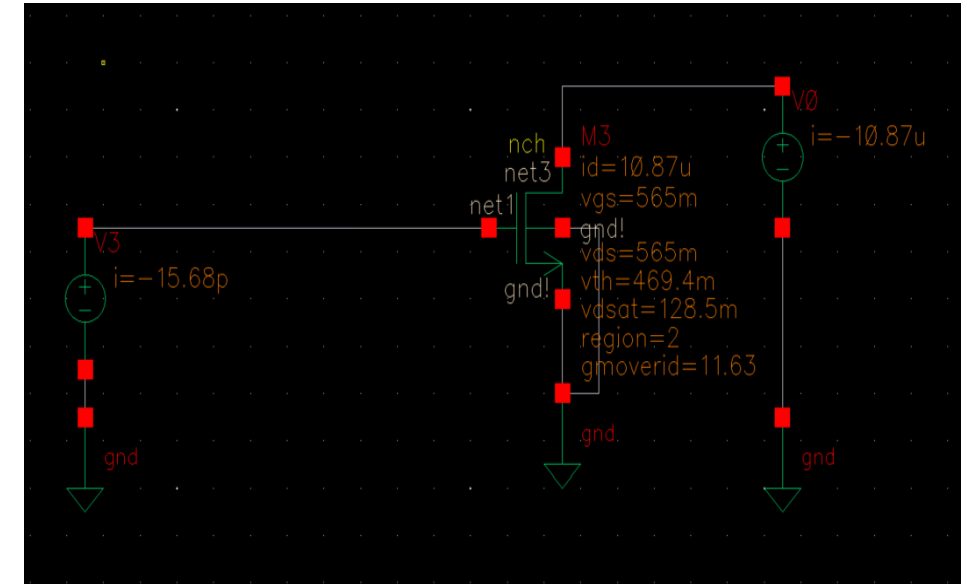We need  $i_d = 100\mu A$ . We slightly increase  $V_{GS}$  to achieve the desired value



DC operating points of M2 as  $ID = 10\mu A$

We design M1 of basic current mirrors with  $V_{DS1} = V_{GS1} = V_{GS2} = 565mV \rightarrow$  Run DC operating points & observe drain current  $\rightarrow$   $gm/i_d$ , JD  $\rightarrow$  Adjust width to the correct value. Width M2 =  $11.5\mu m$

# Experiment 1

ADE L (10) - TQUOC report1 schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Calibre Help cadence

Design Variables

Name	Value
1 finger_nmos	1
2 finger_pmos	1
3 length_M4	1u
4 length_M5	1u
5 width_M4	131.5u
6 width_M5	11.5u
7 length_nmos	60n
8 length_pmos	60n
9 width_nmos	133.6u
10 width_pmos	1.303u
11 vin	100m
12 VINP	486m

Analyses

Type	Enable	Arguments
1 dc	<input checked="" type="checkbox"/>	t
2 ac	<input checked="" type="checkbox"/>	1 10G Automatic Start-Stop

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1 Gain	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>	


Plot after simulation: Auto Plotting mode: Replace

Frequency response of differential pair with diode-connected


Replacing the current source  $I_{SS}$  with a basic current mirror, will provide stability and improve headroom. A current mirror can cause some issues at high frequencies due to factors such as gate-drain capacitance  $C_{gd}$  and gate-source capacitance  $C_{gs}$ . The capacitance of the

State: spectre\_state1

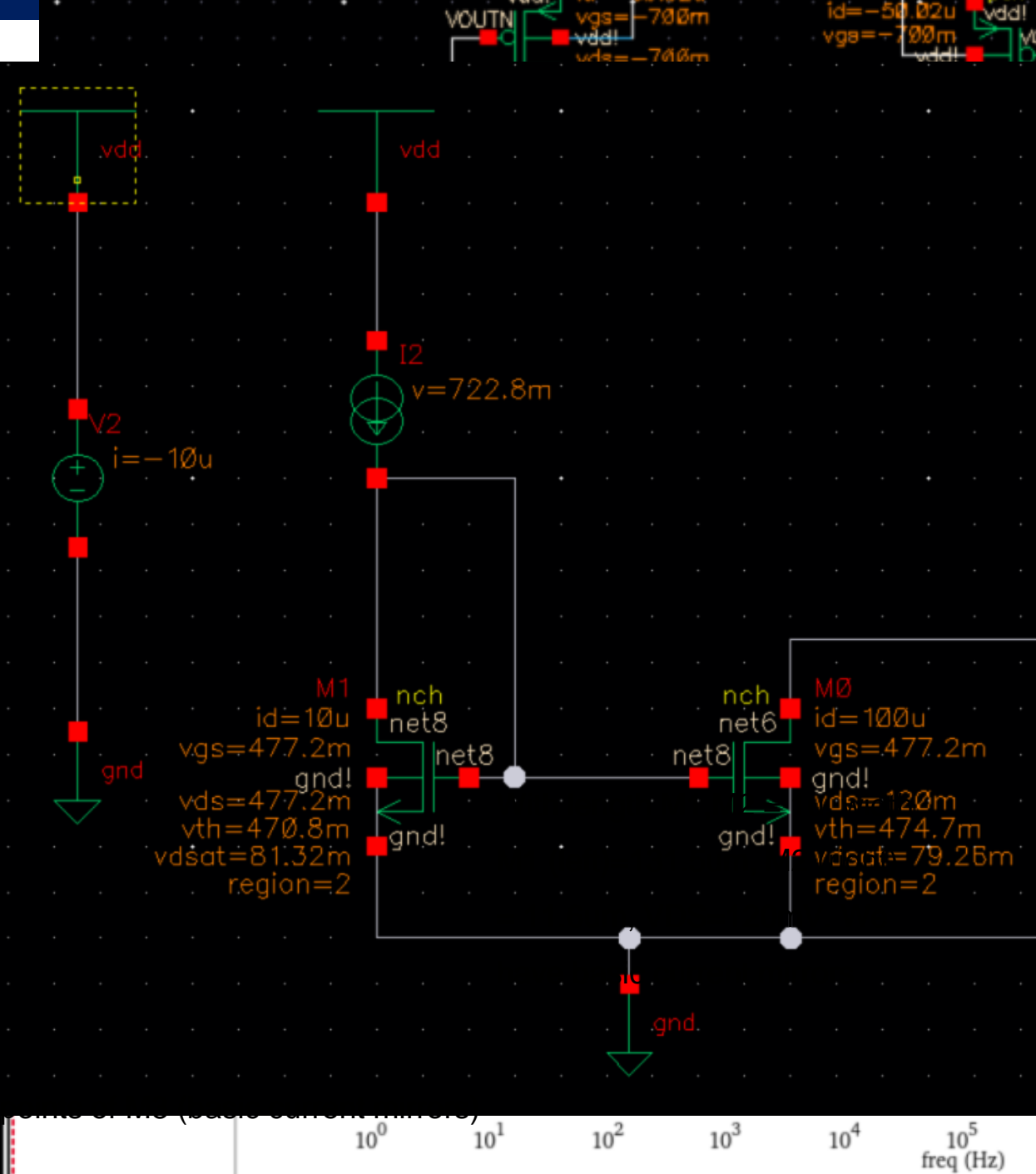
$v_{th}=470.8m$   
 $v_{dsat}=81.32m$   
region=2



 *Compare this structure to the differential pair with current source loads.*



*Diode-Connected Load*

 

*Current Source Load*

**Diode-Connected Load:** A higher gain with a diode-connected load will reduce the output bandwidth due to the requirements for overdrive voltage and the threshold voltage of the transistors. Diode-connected loads typically require lower headroom but can encounter issues when  $V_{out}$  is low, as variations in  $V_{out}$  directly affect the operation of the circuit. Larger overdrive voltages for transistors in a diode-connected load lead to limitations on the output swings.

**Current Source Load:** A circuit with a current source load can achieve higher gain due to the higher output impedance provided by the current source. The stability of the current and better adjustability contribute to increased gain of the circuit. A current source load can provide better and more stable headroom when  $V_{out}$  changes. This is because the current is more stable and less affected by fluctuations in the supply voltage. A circuit with a current source load offers higher gain but lower bandwidth.

# Experiment 2

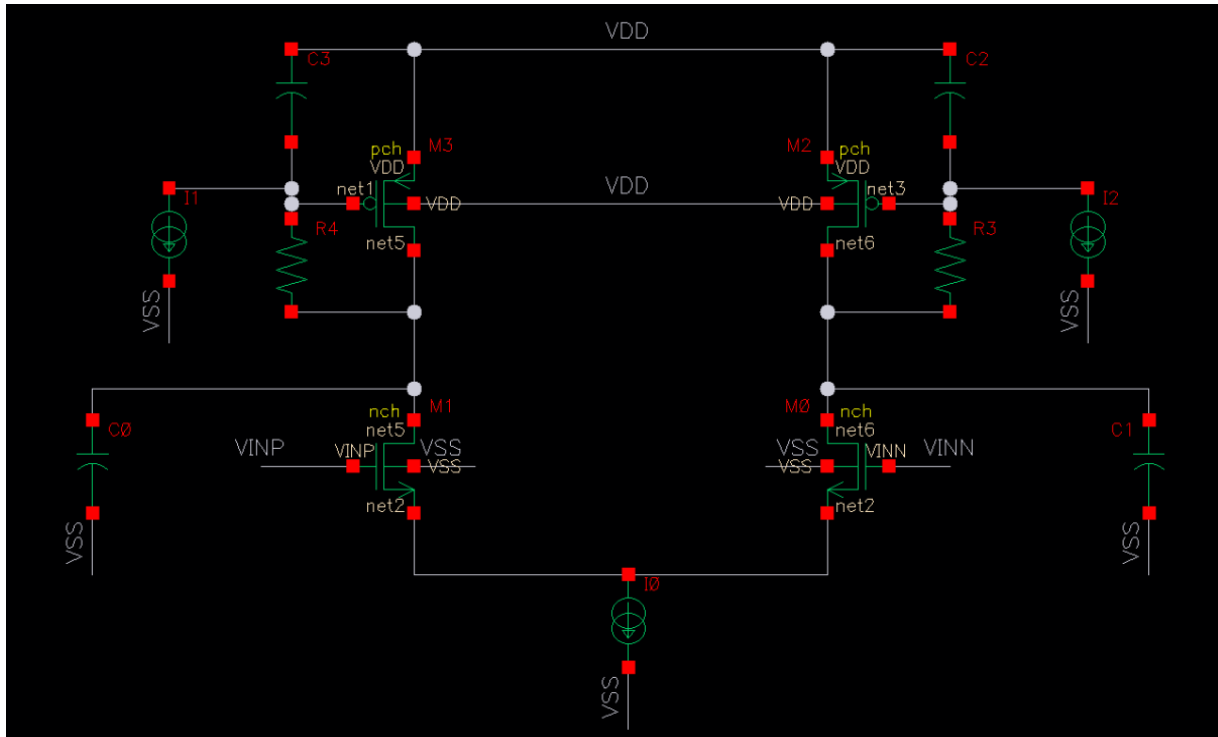


Fig.1 Differential pair with PMOS source follower

Keeping the same components size and value of the previous experiment, we reconfigure the architecture from PMOS diode-connected to a PMOS source follower to increase the bandwidth of our amplifier

## Requirements:

- Find the suitable value for capacitor (C2 & C3), resistor (R3 & R4) and current source (I1 & I2) to achieve a greater UGBW, prove and explain your answer
- What is the trade-off when achieve a wider UGBW


Note: you can refer this link

[https://www.seas.ucla.edu/brweb/papers/Journals/BR\\_SSCM\\_2\\_2020.pdf](https://www.seas.ucla.edu/brweb/papers/Journals/BR_SSCM_2_2020.pdf) to achieve for the value above

 
# Experiment 2

- First, we run the parameter with the values of R searched for with the largest unity gain bandwidth, we choose R. Based on the formula with PMOS  $R_{1.11} = V_{TH}$ , which makes the gap not decrease too much.

$$I_1 R_1 = V_{TH} \Rightarrow I_1 = \frac{529.9m}{100K} = 5.299\mu A$$




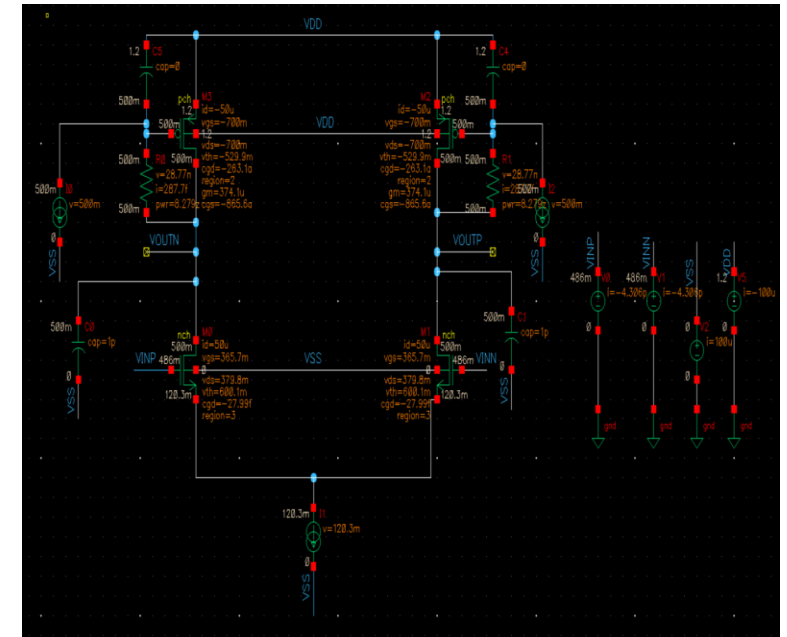Frequency response of Differential pair with PMOS source follower



DC operating points

# Experiment 2

 

As unity gain bandwidth  $\approx 167MHz \Rightarrow \frac{1}{2\pi R_1 C_0} = 167MHz \Rightarrow C_0 = 19.29f$


We have 2 poles and 1 zero point as shown, use the formula to find the points:

As  $C_2 \neq 0$ ;  $C_2 = C_{gd}$ ;  $C_1 = C_{gs} + C_0$

$$f_z = \frac{1}{R_1(C_1 + C_2) \times 2\pi} = \frac{1}{100K(19.29f + 865.6a + 263.1a) \times 2\pi} = 77.95MHz$$

$$f_{p1} = \frac{1}{R_1 C_2 \times 2\pi} = \frac{1}{100K(263.1a) \times 2\pi} = 1.76GHz$$
 
$$f_{p2} = \frac{gm}{C_1 \times 2\pi} = \frac{345u}{19.29f \times 2\pi} = 17.1GHz$$



Input impedance

We see on the plot of  $A_v$  and  $Z_{in}$  that the poles and zeros are quite similar to the theory. With  $Z_{in}$ , when encountering a zero at low frequency,  $Z_{in}$  will increase. Then, when encountering a pole at high frequency,  $Z_{in}$  will decrease by an amount, and at very high frequency,  $Z_{in}$  will decrease to a fairly low level.



# Experiment 2


In theory, the active conductor creates a shunt peaking phenomenon, with 1 capacitor and 1 resistor in parallel at the gate. The purpose is to prevent  $A_v$  from being reduced too much, and to expand the band-width of the circuit.

At low frequencies,  $C_1$  is open so M1 is like a connected diode, at which time  $Z_{in} \approx \frac{1}{g_m}$ ; at high frequencies  $Z_{in}$

increases with frequency, if  $\frac{1}{g_m} \ll R_1 \Rightarrow Z_{in} \approx R_1$

We also run parametric with values  $C_1 = 0 \rightarrow 1p$ . It shows that at low frequencies,  $C_1$  does not affect the gain, however at high frequencies, the larger  $C_1$ , the gain increase higher as meet zero of  $C_1$ .

 The larger the unity band-width, however, the gain decreases quite quickly.



Frequency response of *differential pair with diode-connected* as  $C_1$  changes

# Thank you